



# CSC258: Computer Organization


## Transistors

# Review


- Example: Create an expression that is true if the variables A and B are true, or C and D are true.

$$G = (A \ \& \ B) \ | \ (C \ \& \ D)$$

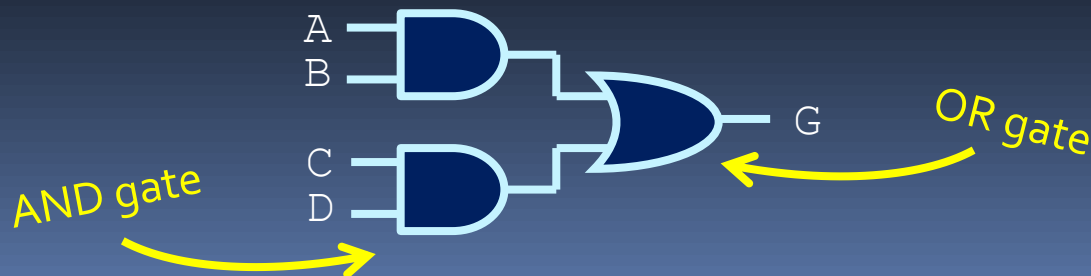- Now create a circuit that does the same thing:




# The course at a glance

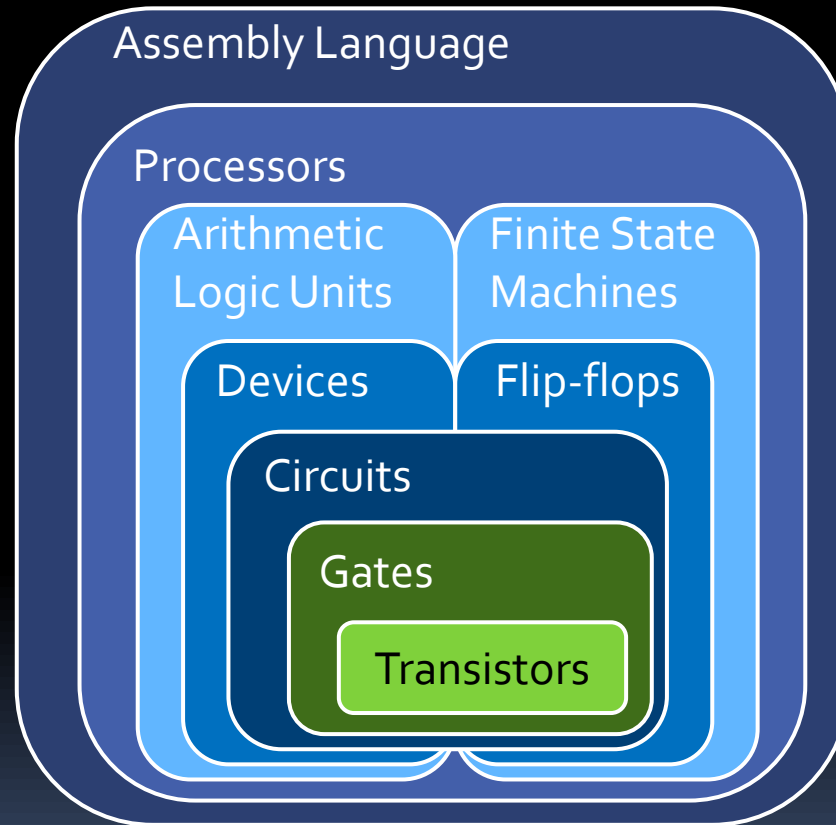

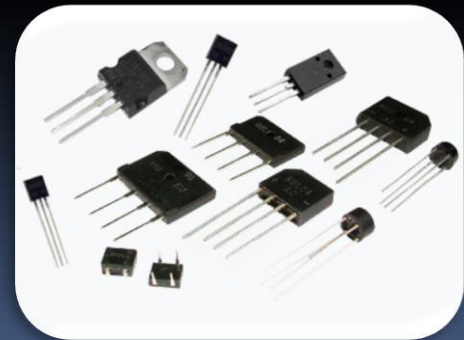
# Starting from the bottom

- Gates can combine values together like logical operators in C or Java.
- But how do gates work?
  - First, we need to understand electricity.
  - Then, we need to understand **transistors**.






# Electricity Basics

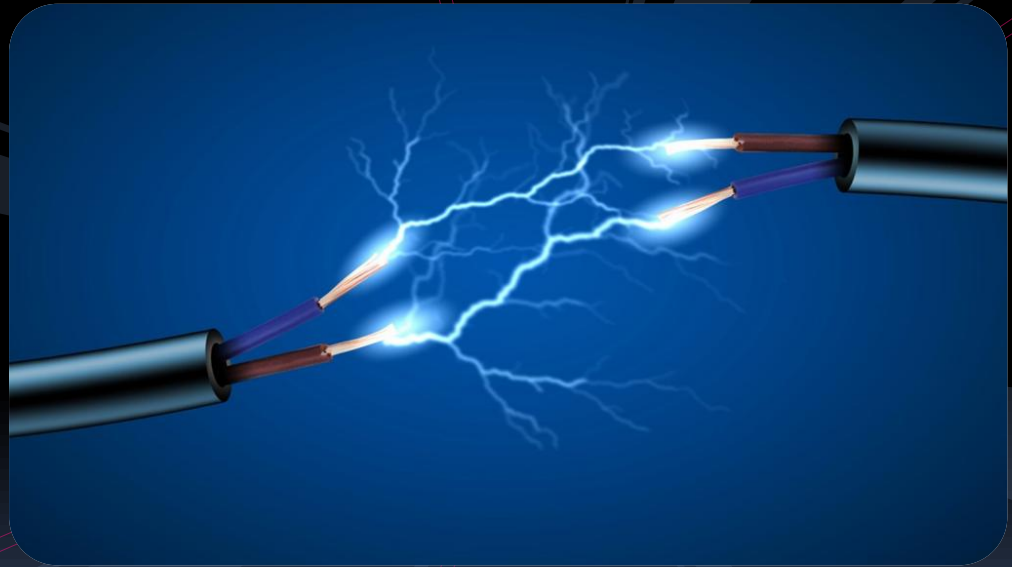


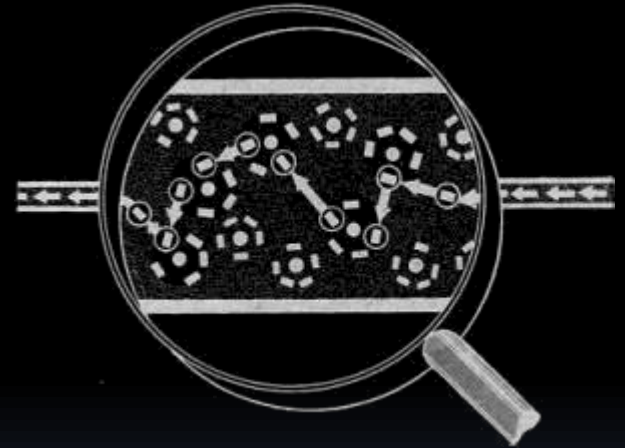
# Intro to Electricity

- Electric current is the flow of charged particles (usually electrons) through a material.
  - Electric current could also be caused by the flow of protons or ions, but this is less relevant for this course.



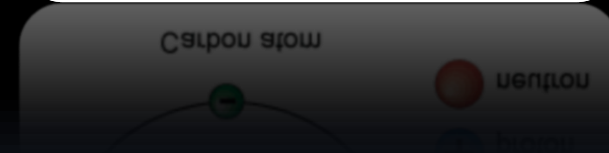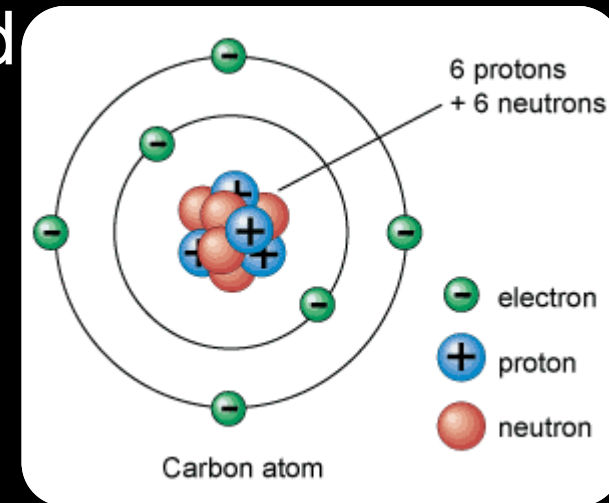
# Electricity = electrons

- Electrons are negatively charged particles
- Protons are positively charged particles
- Particles of the same polarity experience repulsion
- Particles of the opposite polarity experience attraction
- When material (e.g. atom) has equal number of electrons and protons it is electrically neutral


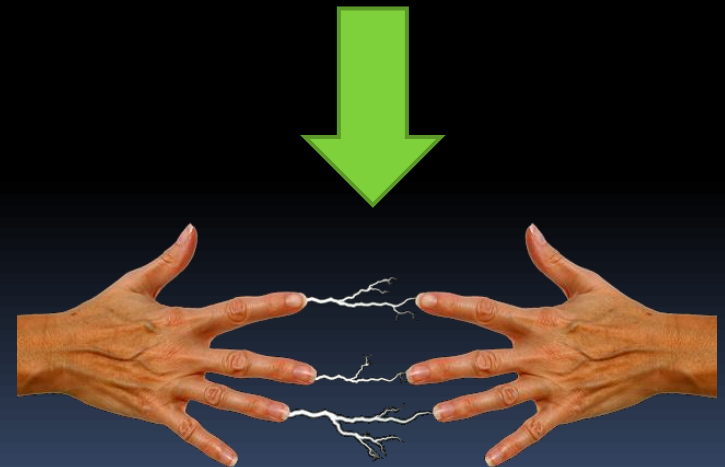
# Static electricity example

- When you shuffle your feet back and forth on a carpet, you pick up extra electrons in your body and develop an electrical imbalance, relative to the ground.
- When you touch an object or person who is electrically balanced, those extra electrons transfer over to that object or person.





# Van de Graaff Generator




# Voltage and current

- Any charged particle produces an electric field in its surrounding
- If one object has more electrons than protons, and another object has fewer electrons than protons, connecting the two causes electrons to flow such that the difference is neutralized
- The two objects have different \_\_\_\_\_
  - Similar to gravitational potential
- The difference in electric potential between two objects is referred to as \_\_\_\_\_
- The rate of flow of electrons when the two objects are connected is called the \_\_\_\_\_

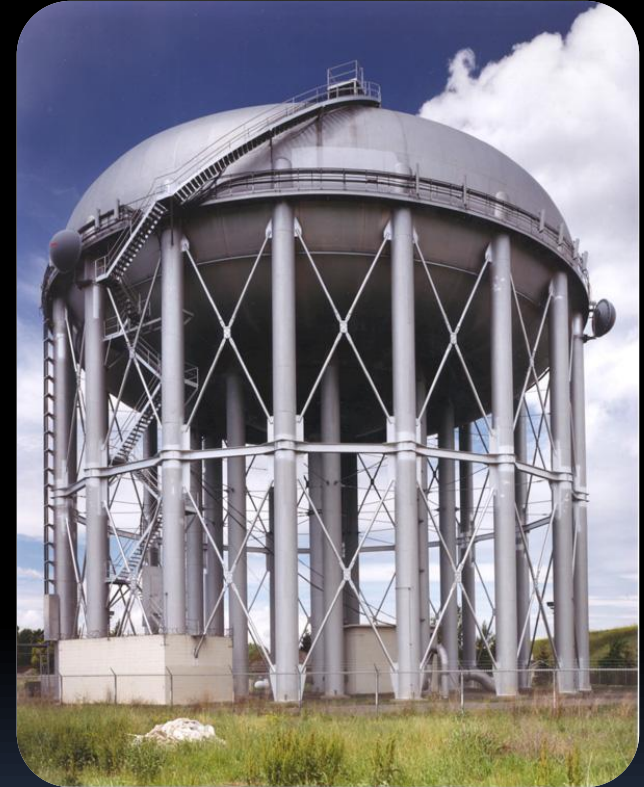
# Water Analogy

- To help picture this concept of voltage and current, imagine a reservoir:
  - Electrons flow from high concentration of electrons to low concentration like water would flow from the reservoir to the ground.
  - Voltage is like the elevation of the water above the ground.
  - Current is the rate at which the water flows.



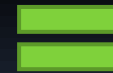
# Sources of electricity

- Where do these electrons (and this electricity) come from?
- Two common sources:
  - Batteries have a concentration of particles stored inside them up that will run out eventually (like water reservoirs).
  - Most electricity that we use comes from electrical outlets, that are constantly being supplied with electric particles that never run out (like waterfalls).


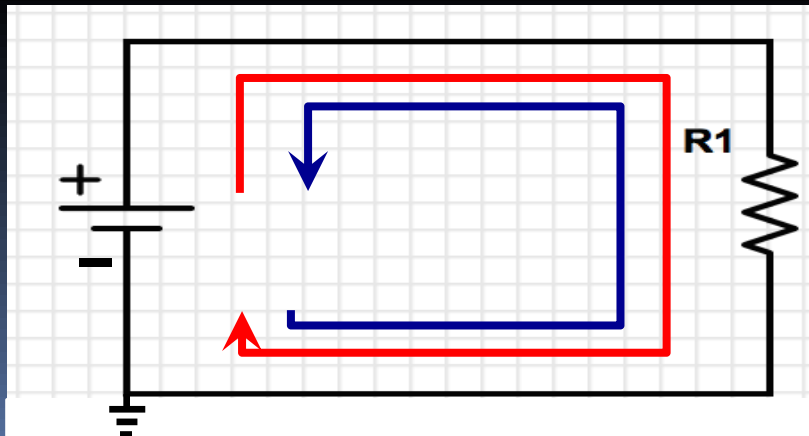
# The path of electricity

- In electric circuits, it is very useful to define a reference point that all other voltages are expressed against:
  - This point is known as zero voltage point of a circuit.
    - Commonly referred to as **ground**.
  - As a convention, current is always said to flow towards ground
    - This is actually opposite direction of the flow of electrons
    - Don't let this confuse you; it's just a convention




## Legend

Electron  
Flow

Current
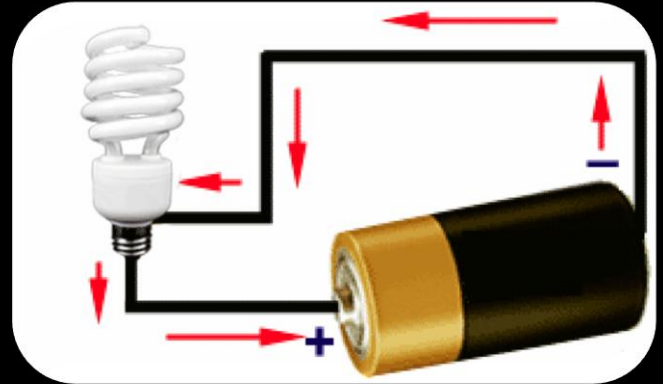
# Using electricity

- Knowing that electric particles want to travel from areas of high concentration to areas of low concentration, we can use this to drive **circuits**.
  - Each circuit has a **source** of electrical particles, some **path** between this source and the ground, and some **resistance** along this path that dissipates the energy from the source.



# Ohm's Law

- The relationship between voltage ( $V$ ) and current ( $I$ ) is called **resistance**
- $R = V/I$
- $I = V/R$ 
  - Given constant resistance, increasing voltage (potential) increases current (flow)

# Resistance is Futile

- In the water analogy, **resistance** would be measure how restrictive the pipe is that connects the reservoir to the ground.
  - Wide, smooth pipe = low resistance
  - Narrow, twisty pipe = high resistance
- Electrical resistance indicates how well a material allows electricity to flow through it:
  - Resistance measured in ohms ( $\Omega$ ). More ohms, more resistance.
  - **Insulators** have high resistance and don't conduct electricity at all, or only under special circumstances.
  - **Conductors** have low resistance and conduct electricity well. Wires usually made of conductive material.




# Semiconductors

- Semiconductor are materials that straddle the boundary between conductors and insulators
- Behave like insulators or conductors, depending on factors like
  - \_\_\_\_\_
  - \_\_\_\_\_
- Example: silicon (Si)



# Transistors

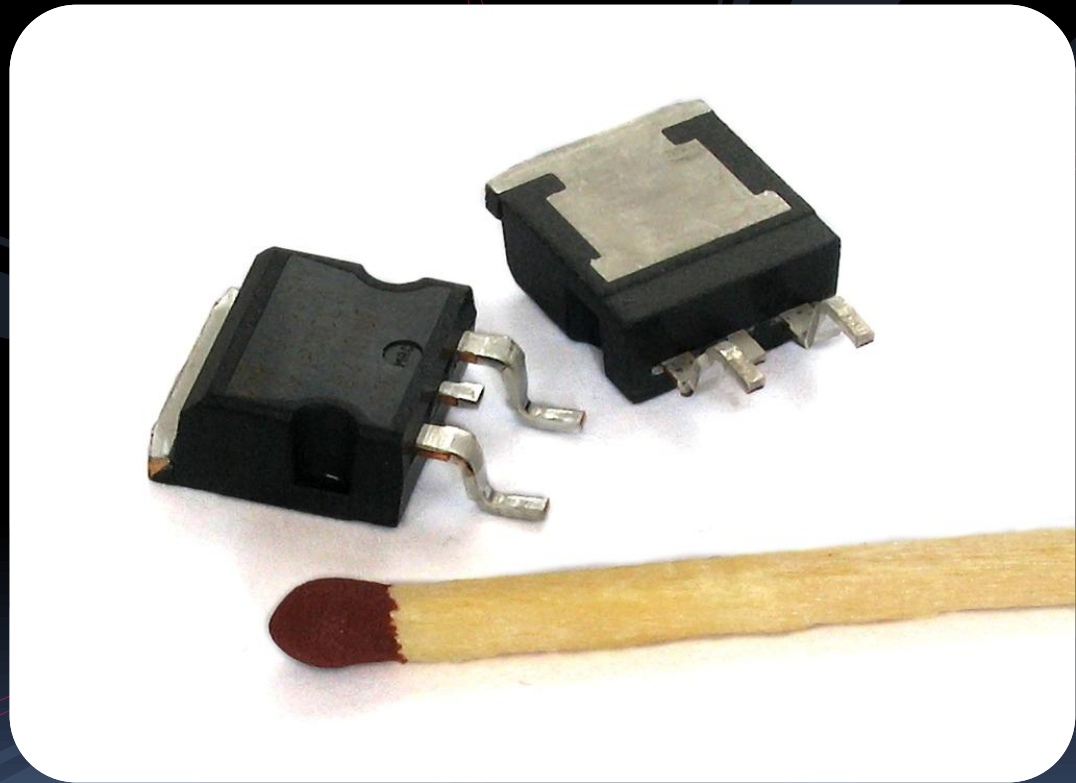


# Introduction to Transistors

- **Transistors** form the basic building blocks of almost all computer hardware.
- Invented by William Shockley, John Bardeen and Walter in 1947, replacing previous vacuum-tube technology.
  - Won Nobel Prize for Physics in 1956.
- Used for applications such as amplification, switching and digital logic design.



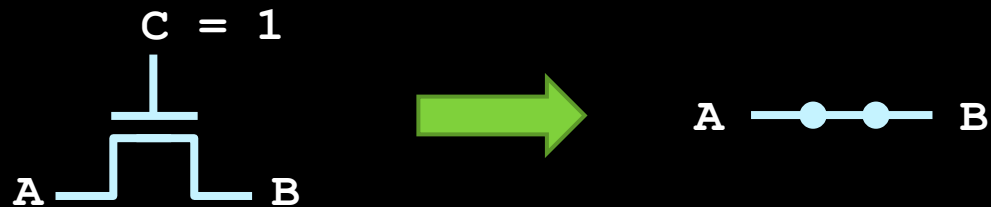
# What do transistors do?

- Transistors connect Point A to Point B, based on the value at Point C.
  - If the value at Point C is high, A & B are connected.



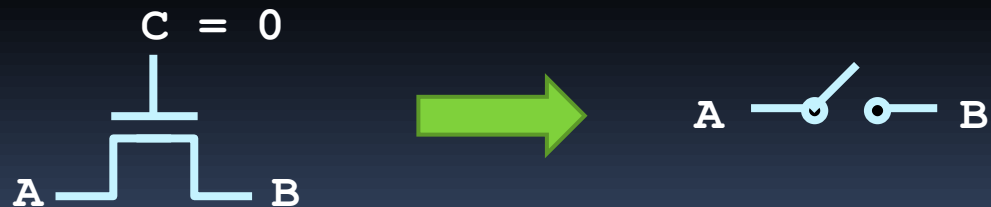
- If the value at Point C is low, A & B are not connected






# Creating transistors


- Transistors use the characteristics of semiconductors to implement useful behaviours, such as amplification and switching.
  - Several different types of transistors exist
  - We will only discuss **MOSFET**
- 

# The MO of MOSFETs

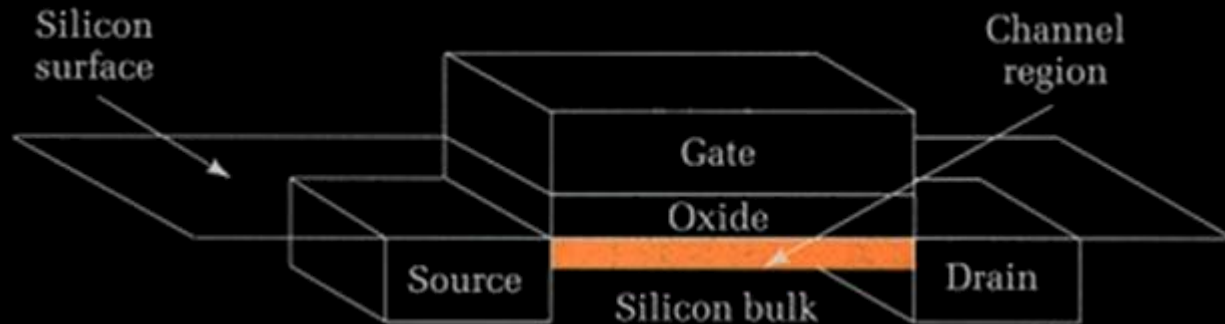

- **Metal Oxide Semiconductor Field Effect Transistors** are composed of a layer of semiconductor material, with two layers on top of the semiconductor:
  - A **m**etal layer (called the gate), that can have an electric charge applied to it
  - An **o**xide layer that doesn't conduct electricity



# Electrodes

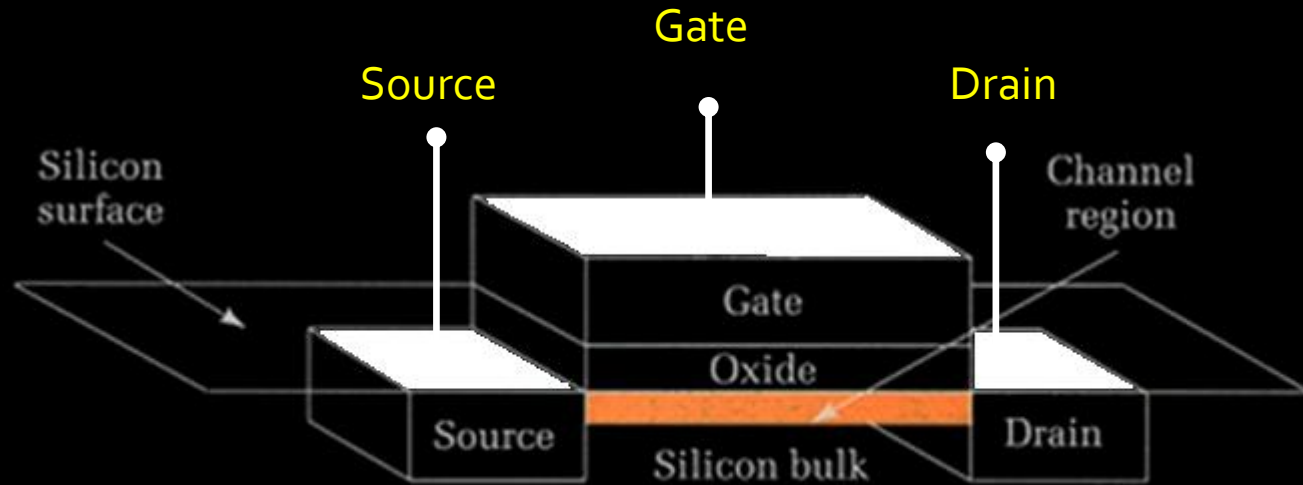

- Due to properties of semiconductors comprising the transistor, channel region does not conduct electricity unless appropriate voltage is applied to the gate
  - The “appropriate” voltage depends on transistor type
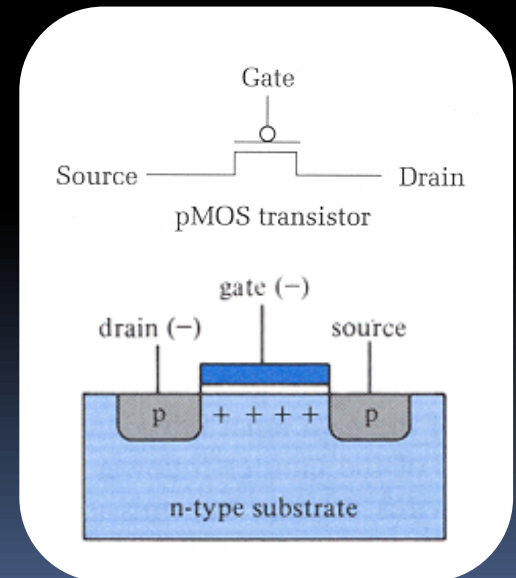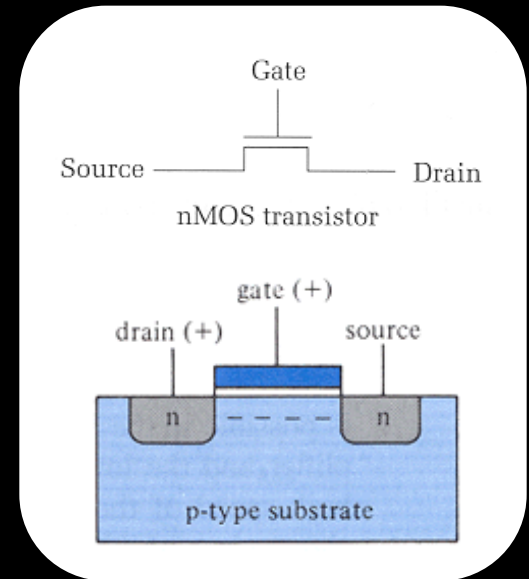
# nMOS vs pMOS

- Two different types of MOSFETs exist, based on the type of semiconductor in the drain and source.
- nMOS conducts electricity between source and drain when positive voltage (5V) is applied to the gate
- pMOS conducts electricity between source and drain when ground (0 V) is applied to the gate






# Making gates

- We can combine nMOS and pMOS transistors to create gates
- Simplest gate is the NOT gate
- By combining nMOS and pMOS, both output 1 and output 0 are guaranteed to be at desired logic level


A	Y
0	1
1	0




# NAND gate

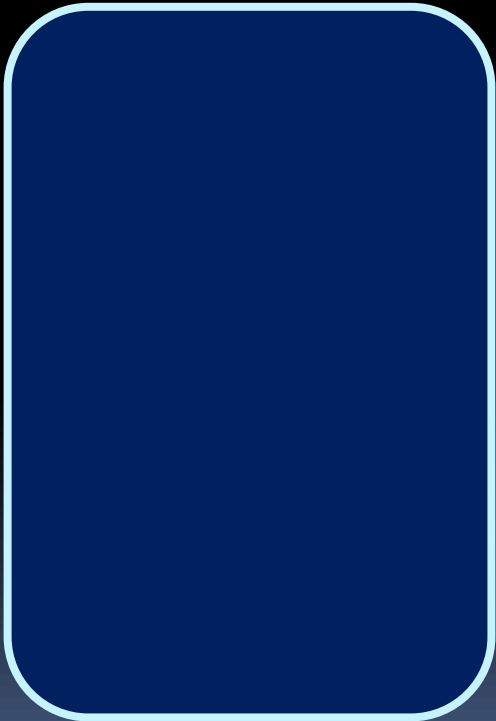


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

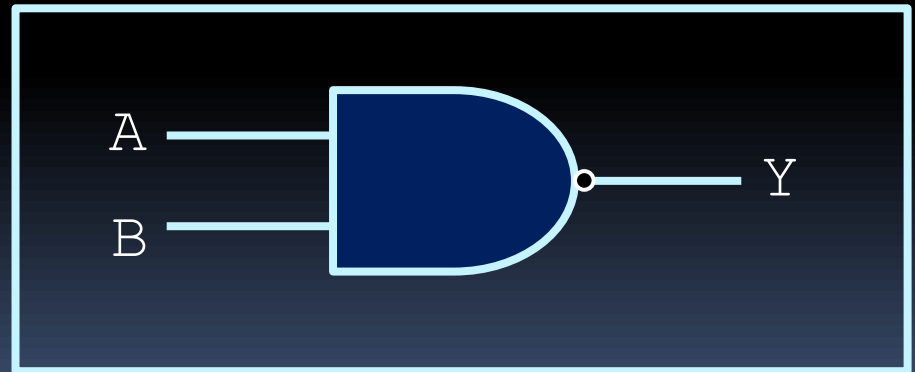

# AND gate?

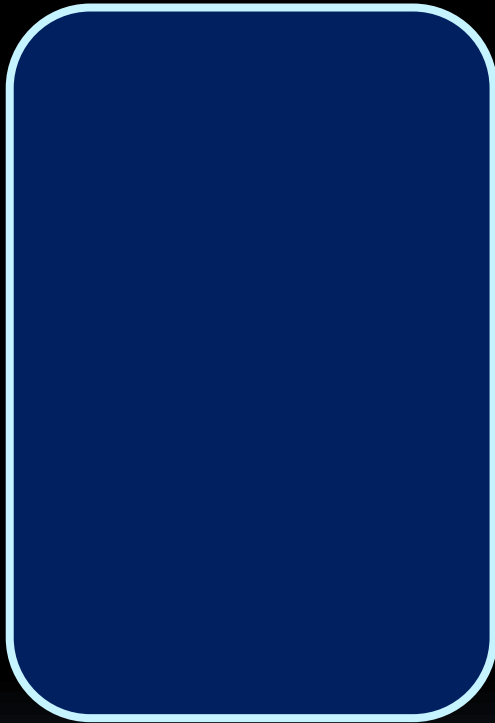


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

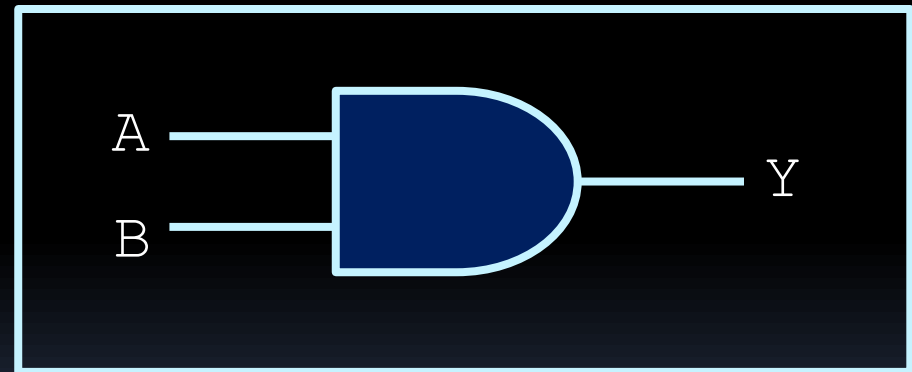



# And gate (the right way)

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

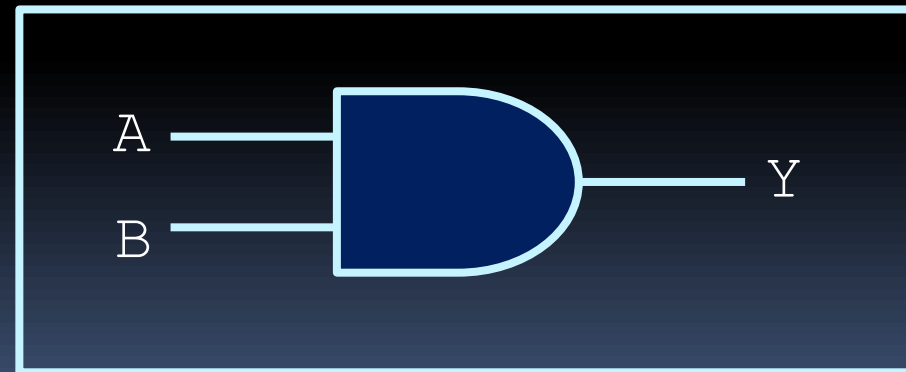
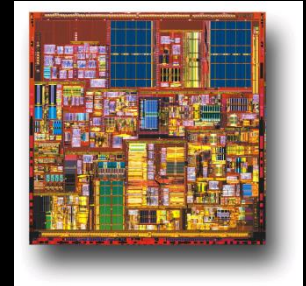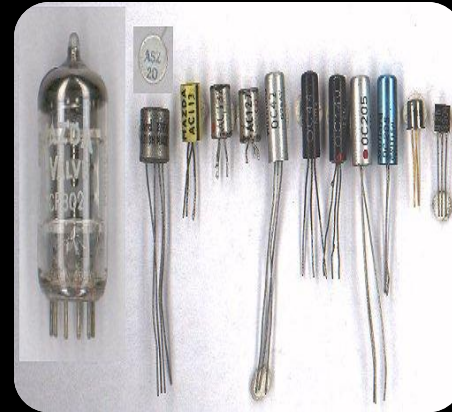
# Transistor/chip Fabrication


- Large numbers of transistors are commonly placed on a single chip
- Chips are made by bombarding silicon with doping substances (impurities) to create the required semiconductor and metal layers
  - Surface is protected between stages to ensure that only the necessary sections are doped.



Watch for more: <https://www.youtube.com/watch?v=aWVywhzuHnQ>




# Creating circuits with gates

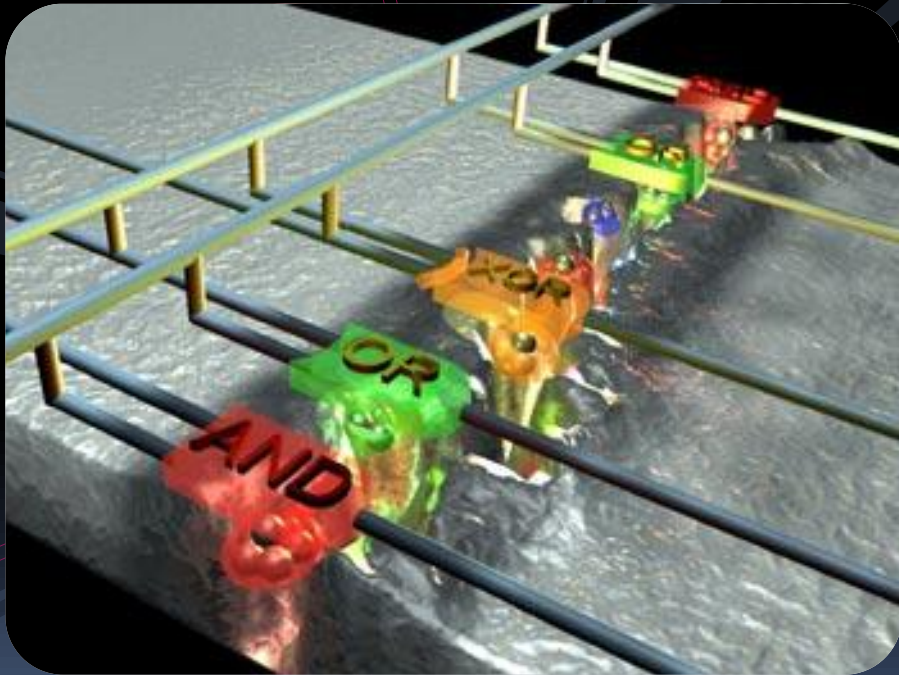


# More common gate types

## NAND

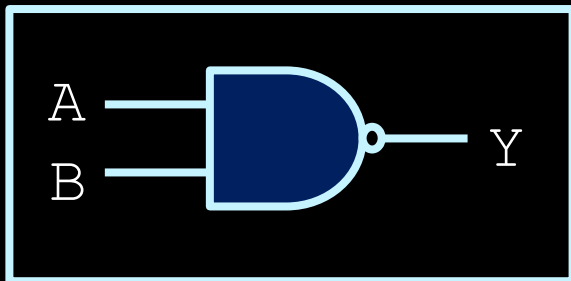


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

## NOR

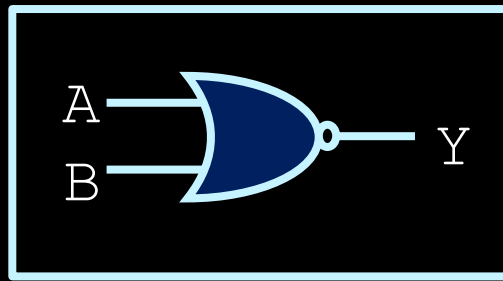

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

## XOR

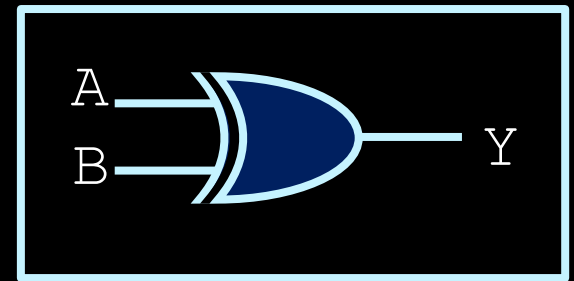


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

# Implementing Boolean expressions

- How to implement Boolean expressions using logic gates?

$$Y = (A \text{ or } B) \text{ and } (\text{not } A \text{ or not } B) \text{ or } C$$

- Like so:

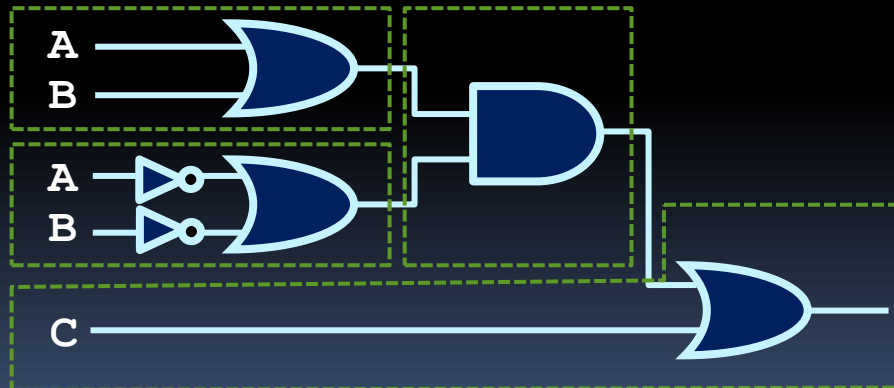




# The Big Picture

- What are Boolean expressions good for?
- Controlling a robot
  - $\text{Stop} = \text{BatteryLow} \text{ OR } \text{ObstacleDetected}$
  - $S = B \mid D$
- Mars rover
  - $\text{Turn Left} = (\text{ObstacleAhead} \text{ AND } \text{ObstacleRight} \text{ AND not } \text{ObstacleLeft}) \text{ OR } \text{AlienLeft}$
  - $T_L = (O_A \& O_R \& !O_L) \mid A_L$

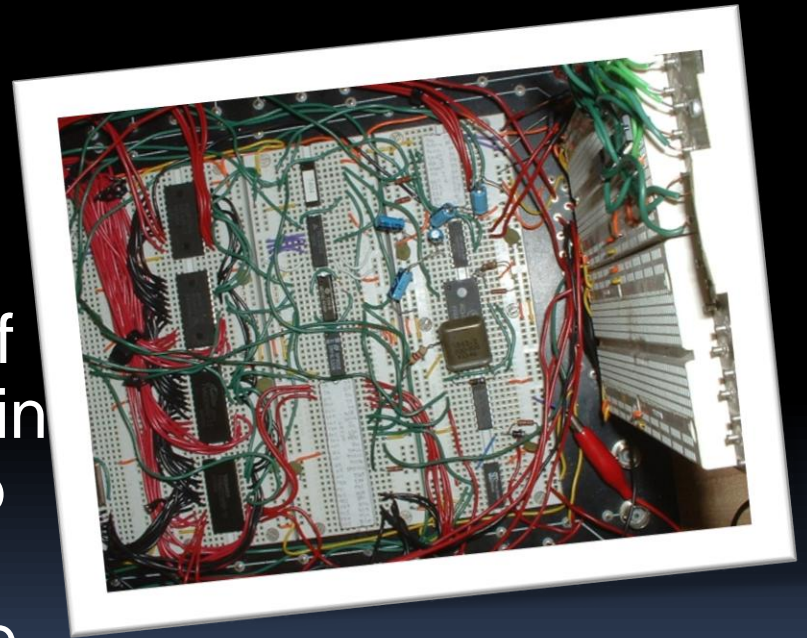
# Creating complex circuits

- What do we do in the case of more complex circuits, with many inputs and more than one output?
  - If you're lucky, a truth table is provided to express the circuit.
  - Usually the behaviour of the circuit is expressed in words, and the first step involves creating a truth table that represents the described behaviour.


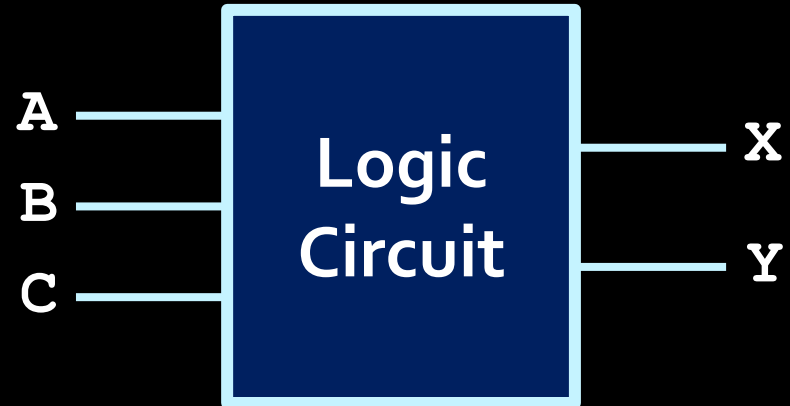
# Circuit example



- The circuit on the right has three inputs (A, B and C) and two outputs (X and Y).



- What logic is needed to set  $x$  high when all three inputs are high?
- What logic is needed to set  $y$  high when the number of high inputs is odd?

# Combinational circuits

- Small problems can be solved easily.

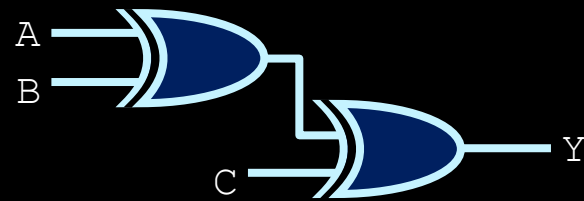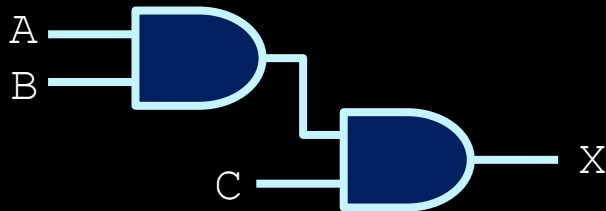

- Larger problems require a more systematic approach.

# Creating complex logic

- How do we approach problems like these (and circuit problems in general)?
- Basic steps:
  1. Create one or more truth tables.
  2. Express as Boolean expression.
  3. Convert to gates.
- The key to an efficient design?
  - Spending extra time on Step #2.


# Example truth table

- Consider the following example:
  - *“Given three inputs  $A$ ,  $B$ , and  $C$ , make output  $Y$  high whenever any of the inputs are low, except when all three are low or when  $A$  and  $C$  are high.”*

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


# Implementation 1

A B C

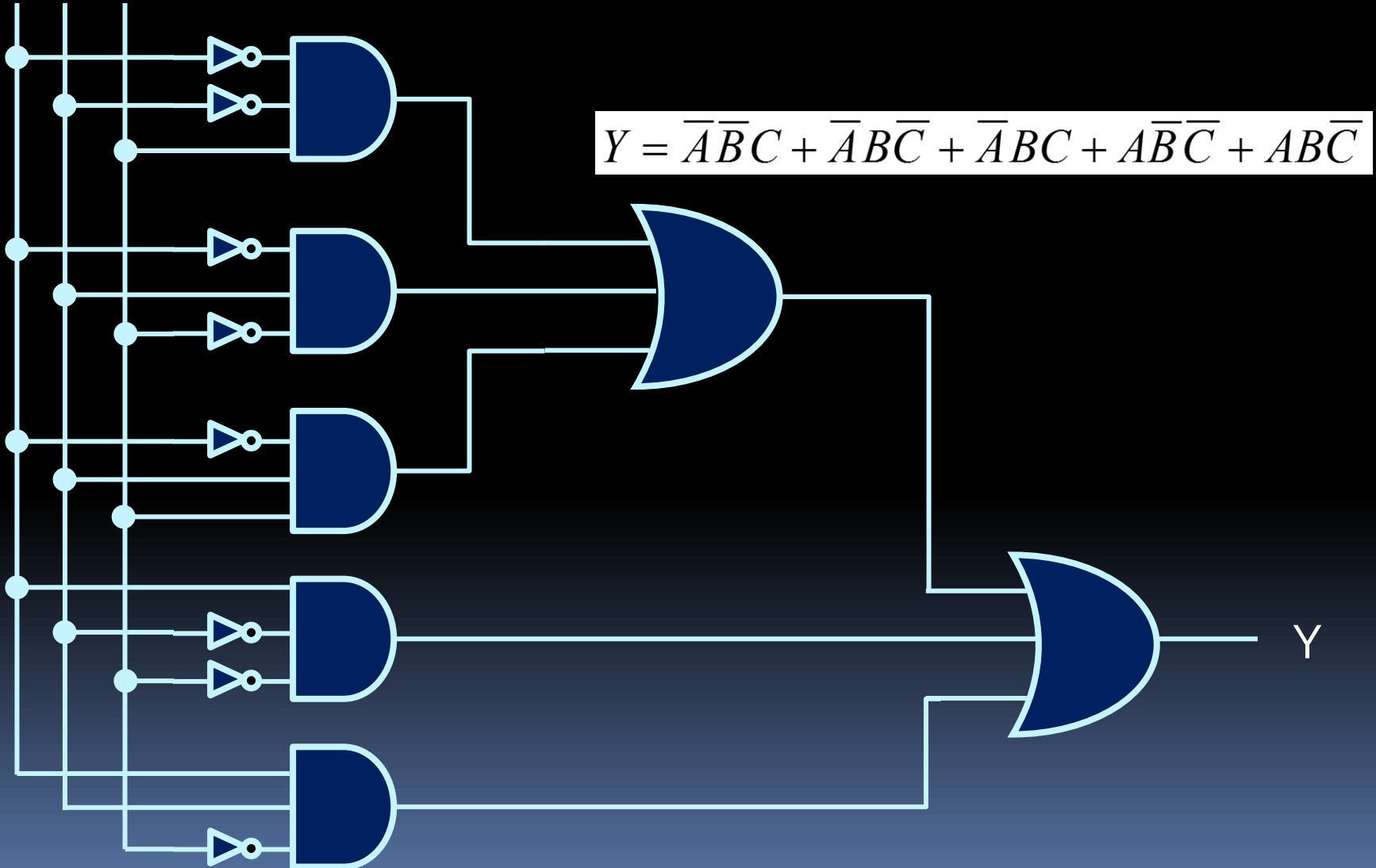

## Implementation 2

A B C

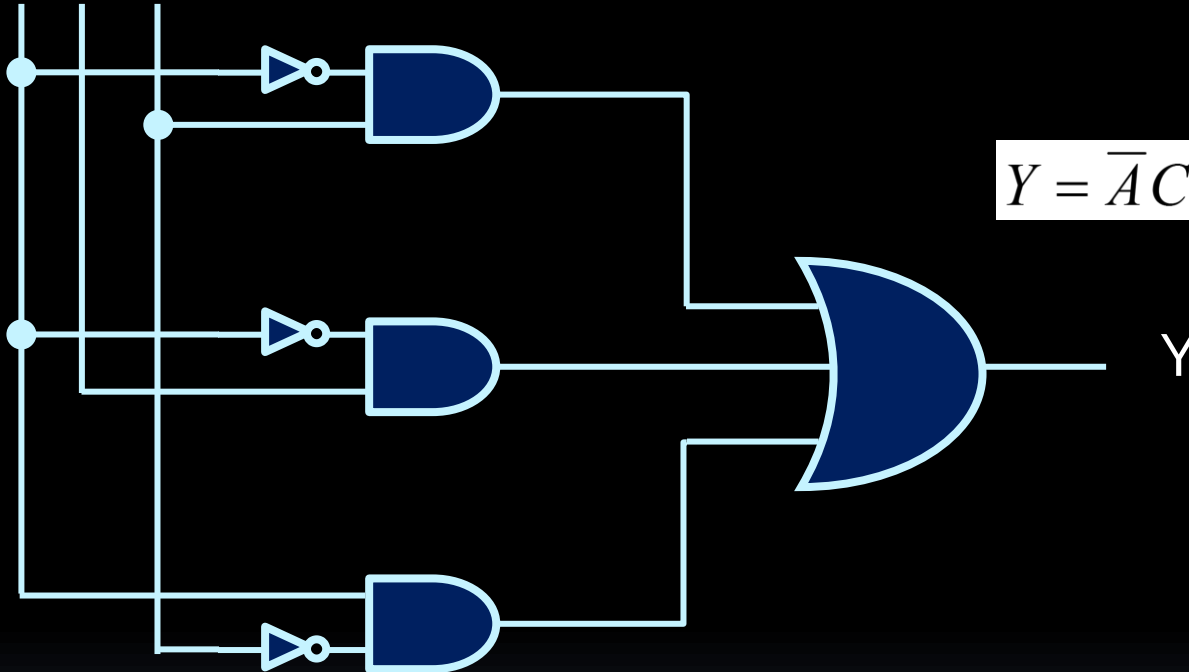

$$Y = \overline{A}C + \overline{A}B + A\overline{C}$$

- Which implementation would you prefer?